 


# Exercise E12



# Exercise E12

$V_S$  and  $V_D$  are mixed up in the initial LTSpice model, so these two values are wrong as well. The errors are left here, serving as a reminder.

## LTSpice Simulation Results:

- $V_S = 2.52V$ ;  $V_D = 0.50V$ ;  $V_G = 2.70V$ ;  $V_{DD} = 5.00V$
- $I_D = 14.9mA$ , and the current floating through  $R_S$ ,  $R_D$ , Source-to-Drain, are all the exact same. (Probably the LTSpice model is just configured to do this?)
- $I_{R1} = I_{R2} = 2.70\mu A$
- No current between Gate and Drain
- Comments: From the values above (after the orange corrections):  $V_{DS} = 2.02V$ ,  $V_{GS} = 2.20V$ ,  $I_D = 14.9mA$ . All these values match very well with the givens, especially considering I only kept four sig figs in the resistances in the simulation. (i.e., 33.33Ohms)